
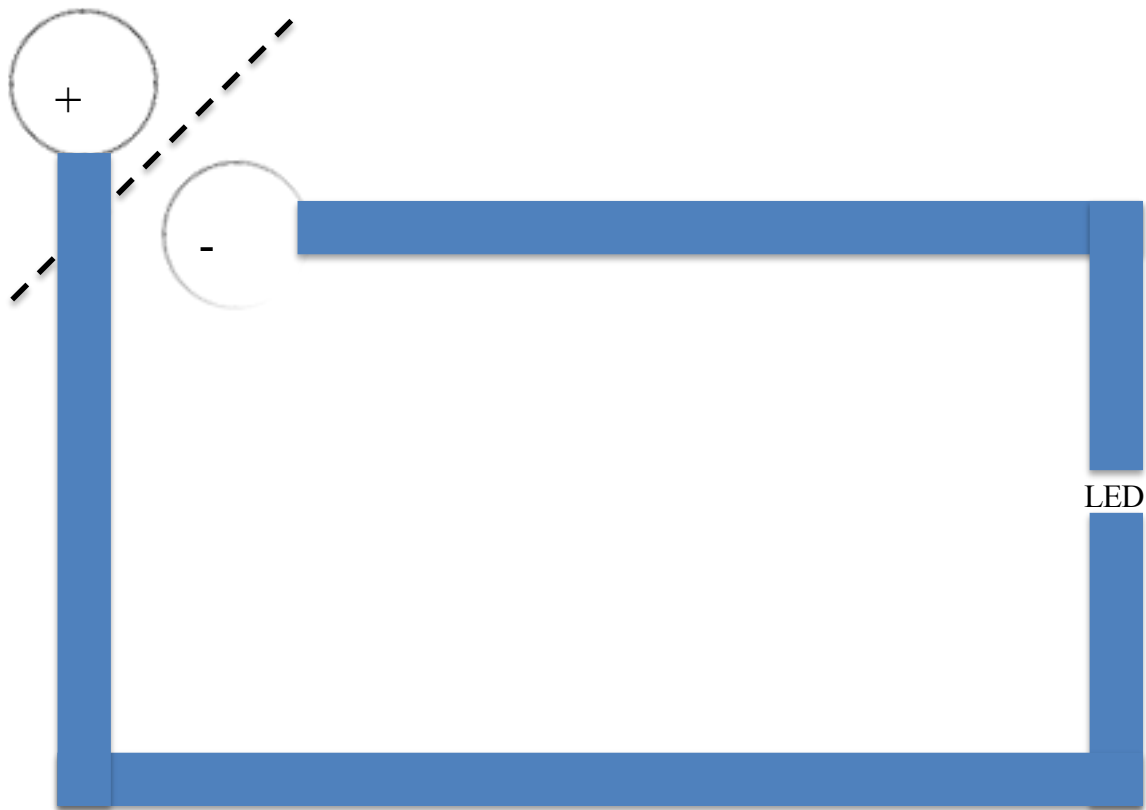


Post Activity – Circuit Templates

Simple Paper Circuit Template

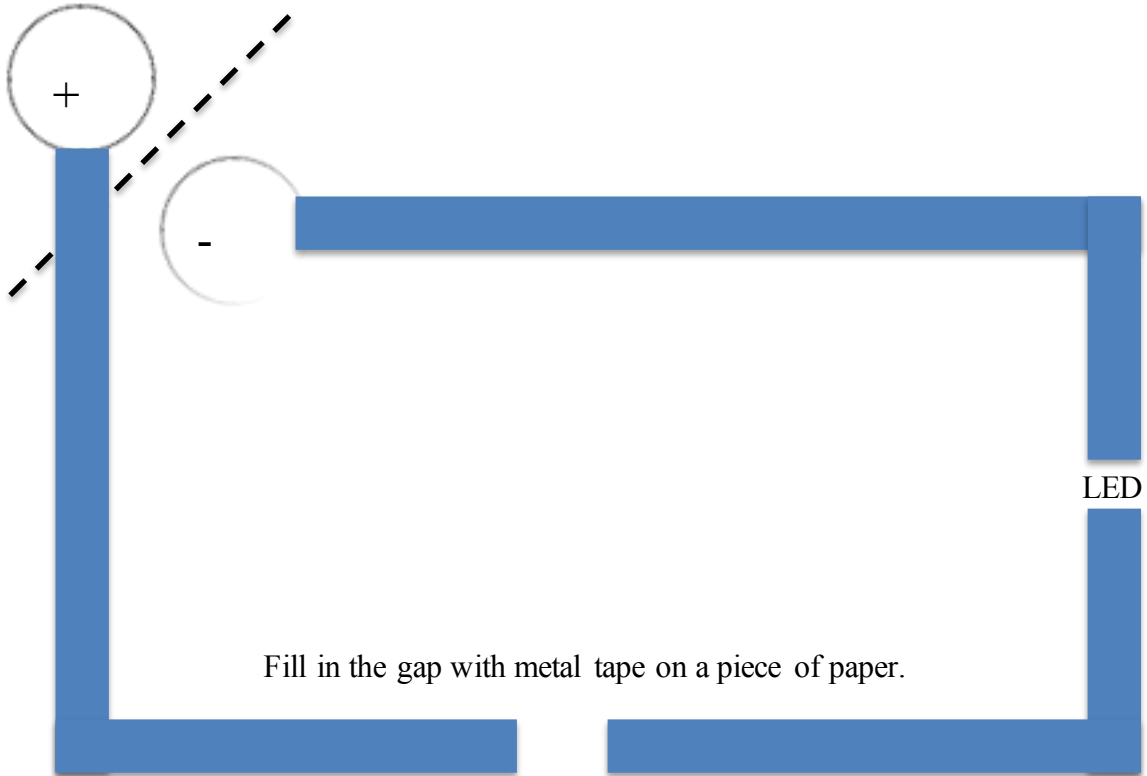


Simple Circuit with Switch



Fill in the gap with metal tape on a piece of paper.

Parallel Circuit

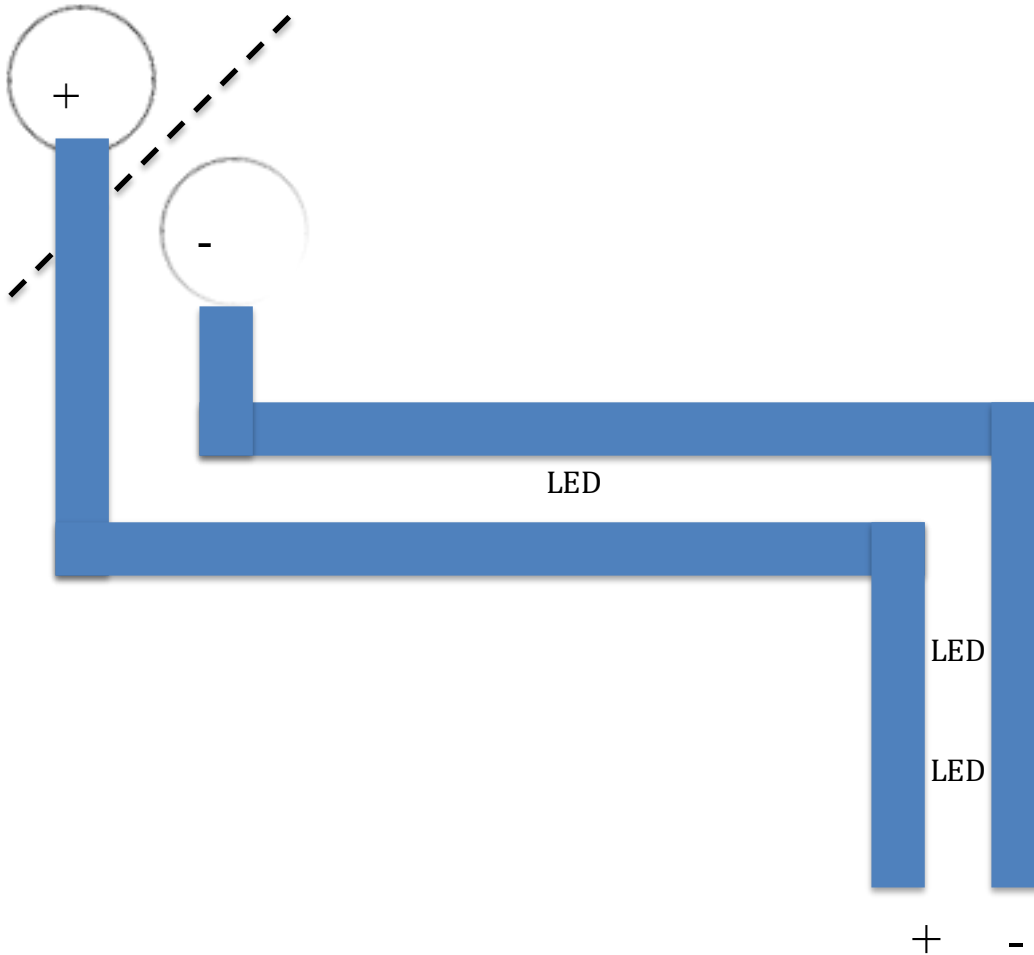

This is a simple parallel circuit. This template could be used to do something like traffic lights that light up with pressure if the LEDs are attached to a separate piece of paper. Search traffic light paper circuit.

Circuit with Blinking Light Slider

